

TED (15/19) -3212  
(Revision- 2015/19)

**A21-09611**

Reg.No.....  
Signature. ....

DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/MANAGEMENT/  
COMMERCIAL PRACTICE – APRIL -2021.

**DIGITAL CIRCUITS**

(Maximum Marks : 75)

[Time : 2.15 hours]

**PART-A**

Marks

**I.** Answer **any three** questions in one or two sentences. Each question carries 2 marks.

1. Define 2's complement of a number with example.
2. State De-Morgan's Theorem.
3. Define Combinational logic.
4. Name the asynchronous inputs of a Flip-Flop.
5. List the various display in digital meter.

(3x2=6)

**PART - B**

**II** Answer **any four** of the following questions . Each question carries 6 marks.

1. Convert

(i)  $100_{10}$  to  $(\quad)_2$

(ii)  $25D_{16}$  to  $(\quad)_2$

(iii)  $01000111_2$  to  $(\quad)_{16}$

2. What is a half adder. Give its truth table. Realize it using any gates.
3. Explain the operation of D flip flop with logic diagram and truth table.
4. Define the terms Resolution and Sensitivity of DAC.
5. Reduce the expression  $F=A+AB+ ABC+ ABCD$ .
6. Draw the circuit of 4 bit asynchronous Up counter using JK Flip Flop along with its truth table.
7. Compare RAM and ROM.

[4x6 =24]

**PART - C**

(Answer **any of the three units** from the following. Each full question carries 15 marks)

**UNIT I**

**III** (a) Draw the logic diagram and truth table of two input NOR gate and EXOR gate. (6)

(b) Solve the following.

- (i)  $1000+1010$       (ii)  $11001-1100$       (iii)  $1.01 \times 10.1$       (9)

**OR**

**IV** (a) Simplify Boolean function  $F(A,B,C,D) = \sum_m (1,2,3,5,6,7,8,10,13,15)$       (9)

(b) Compare weighted and non-weighted code.      (6)

**UNIT- II**

**V** (a) Draw the circuit and explain the working of TTL NAND gate.      (7)

(b) Define the terms (i) Propagation delay    (ii) Noise Margin  
(iii) Fan out    (iv) Fan in      (8)

**OR**

**VI** (a) Explain the working of a 4-to-1 multiplexer. Write its truth table and sketch its logic diagram.      (8)

(b) Describe the operation of 1 bit comparator circuit.      (7)

**UNIT- III**

**VII** (a) Explain the operations of Serial in Parallel out shift register with neat sketch.      (8)

(b) Draw the circuit of Decade counter and give its truth table.      (7)

**OR**

**VIII** (a) Draw and explain the operation of Master Slave J K Flip Flop with its truth table.      (9)

(b) Compare asynchronous and Synchronous counter.      (6)

**UNIT – IV**

**IX** (a) Explain the working of Successive Type ADC with neat sketch.      (8)

(b) Explain the various types of ROM.      (7)

**OR**

**X** (a) Explain the operation of R-2R ladder type DAC converter with neat sketch.      (10)

(b) List the specifications of digital meter display.      (5)