

TED (15/19)-3212  
(Revision-2015/19)

**N21-06430**

Reg.No.....  
Signature. ....

DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/MANAGEMENT/  
COMMERCIAL PRACTICE –NOVEMBER -2021.

**DIGITAL CIRCUITS**

(Maximum Marks : 75)

[Time : 2.15 hours]

**PART-A**

Marks

**I.** Answer **any three** questions in one or two sentences. Each question carries 2 marks.

1. Convert  $(367.52)_8$  to binary.
2. Define fan in of a logic gate.
3. List the asynchronous inputs to a flip flop.
4. Define sensitivity of a digital meter.
5. Define the modulus of a counter.

(3x2=6)

**PART - B**

**II** Answer **any four** of the following questions . Each question carries 6 marks.

1. State Demorgan's theorems.
2. Explain the operation of a Full adder.
3. Illustrate the operation of a edge triggered J-K flip flop.
4. Compare RAM and ROM.
5. Simplify  $f = \overline{(A+\overline{BC})} \cdot (\overline{AB}+ABC)$  using Boolean laws.
6. Implement EX-OR gate using NAND gate.
7. Draw the logic diagram of a serial in parallel out shift register.

(4x6 =24)

## PART - C

(Answer **any of the three units** from the following. Each full question carries 15 marks)

### UNIT I

- III** (a) Solve the following (i)  $(110101.101010)_2 = (\text{-----})_8$  (ii) Multiply  $(1101)_2$  by  $(110)_2$ . (6)  
(b) Reduce the expression  $F = \sum m(0, 1, 2, 3, 6, 7, 13, 15)$  using K-map. (9)

### OR

- IV** (a) Solve the following (i) Divide  $(101101)_2$  by  $(110)_2$  (ii)  $(3A9E.B0D)_{16} = (\text{-----})_2$ . (6)  
(b) Reduce the expression  $F = \prod M(0, 1, 2, 3, 4, 10, 11, 15)$  using K-map. (9)

### UNIT- II

- V** (a) Explain the operation of a TTL NAND gate. (9)  
(b) Illustrate the operation of a 4X1 Multiplexer. (6)

### OR

- VI** (a) Explain the operation of a BCD-Decimal decoder. (9)  
(b) Illustrate the operation of a one bit comparator. (6)

### UNIT- III

- VII** (a) Design a decade asynchronous counter. (9)  
(b) Draw the circuit of a parallel in serial out shift register. (6)

### OR

- VIII** (a) Design a 4 bit synchronous counter. (9)  
(b) Compare synchronous counter and asynchronous counter. (6)

### UNIT – IV

- IX** (a) Explain the operation of a single slope A/D Converter. (8)  
(b) Describe the working of a binary weighted converter. (7)

### OR

- X** (a) Explain the operation of Successive approximation A/D converter. (8)  
(b) Describe the working of a R-2R D/A converter. (7)

\*\*\*\*\*