

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/
MANAGEMENT/COMMERCIAL PRACTICE, NOVEMBER – 2022**

DIGITAL COMPUTER PRINCIPLES

[Maximum Marks: 100]

[Time: 3 Hours]

PART-A

[Maximum Marks: 10]

I. (Answer *all* questions in one or two sentences. Each question carries 2 marks)

1. List two universal gates.
2. Define Combinational Logic Circuit.
3. Draw the circuit diagram for a 2 to 1 multiplexer.
4. Write any two applications of flip flops.
5. List any two type of digital to analog converter. (5 x 2 = 10)

PART-B

[Maximum Marks: 30]

II. (Answer *any five* of the following questions. Each question carries 6 marks)

1. Draw the truth table and logic symbol of NAND and NOR logic gates.
2. Define Minterm and Maxterm with examples.
3. Design and implement a full adder circuit.
4. Simplify using Karnaugh Map $F = \sum m(0,1,3,5,6,9,11,12,13,15)$
5. Show how a JK flip - flop is converted to a T-FF and D-FF.
6. Differentiate between synchronous and asynchronous counters.
7. Explain a Counter type ADC with neat figure. (5 x 6 = 30)

PART-C

[Maximum Marks: 60]

(Answer *one* full question from each Unit. Each full question carries 15 marks)

UNIT – I

- III. (a) Define universal property of NAND gate. Implement AND and OR gates using NAND gates alone. (9)
- (b) Find: (i) Gray code equivalent of binary 1010 (ii) Binary equivalent of 1010 Gray code. (6)

OR

- IV. (a) Draw the symbols and truth tables of EX-OR and EX-NOR gates and explain. (7)
- (b) Convert
- (i) Octal number 632 to hexadecimal (iii) Decimal 32.46 to binary
- (ii) Hexadecimal E0B3 to decimal (iv) Decimal 83 to octal (8)

UNIT – II

- V. (a) Distinguish between decoder and demultiplexer with neat figures. (8)
- (b) Design a circuit for the following function: $F(A,B,C,D) = \Sigma m(1,2,3,5,7,9,10,11,13,15)$ (7)

OR

- VI. (a) State the need of decoders. Design a logic circuit to decode the binary number 1001 for producing HIGH level at the output. (7)
- (b) Design and implement a four bit binary to gray code converter. (8)

UNIT- III

- VII. (a) With truth table and logic diagram explain the working of a JK flipflop. (8)
- (b) Explain the working of a 3 bit asynchronous counter using T Flip Flop with neat diagram. (7)

OR

- VIII. (a) Explain the working of a mode-10 ripple counter with diagram. (8)
- (b) Explain the working of serial in serial out shift register with diagram. (7)

UNIT - IV

- IX. (a) State the DAC Parameters-(offset voltage and Monotonicity, Accuracy and setting time) (8)
- (b) Explain a weighted resistor type DAC with neat figure. (7)

OR

- X. (a) Describe the need of DAC and ADC in digital systems. (8)
- (b) What are the difference between RAM and ROM. (7)
